

6-12 THE INTEGRATOR

A circuit in which the output voltage waveform is the integral of the input voltage waveform is the *integrator* or the *integration amplifier*. Such a circuit is obtained by using a basic inverting amplifier configuration if the feedback resistor R_F is replaced by a capacitor C_F [see Figure 6-23(a)].

The expression for the output voltage v_o can be obtained by writing Kirchhoff's current equation at node v_2 :

$$i_1 = I_B + i_F$$

Since I_B is negligibly small,

$$i_1 \cong i_F$$

Recall that the relationship between current through and voltage across the capacitor is

$$i_c = C \frac{dv_c}{dt}$$

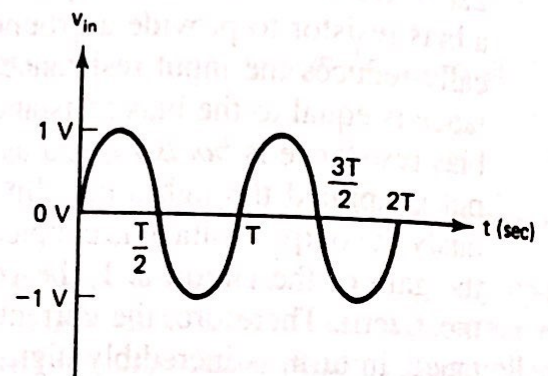
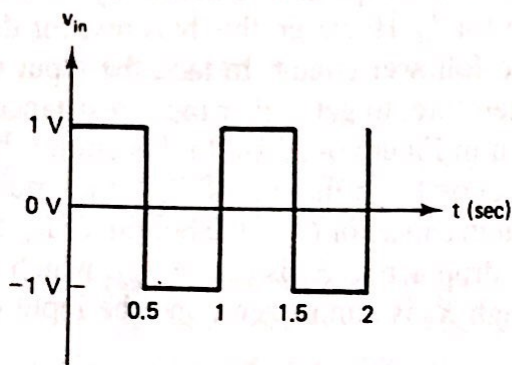
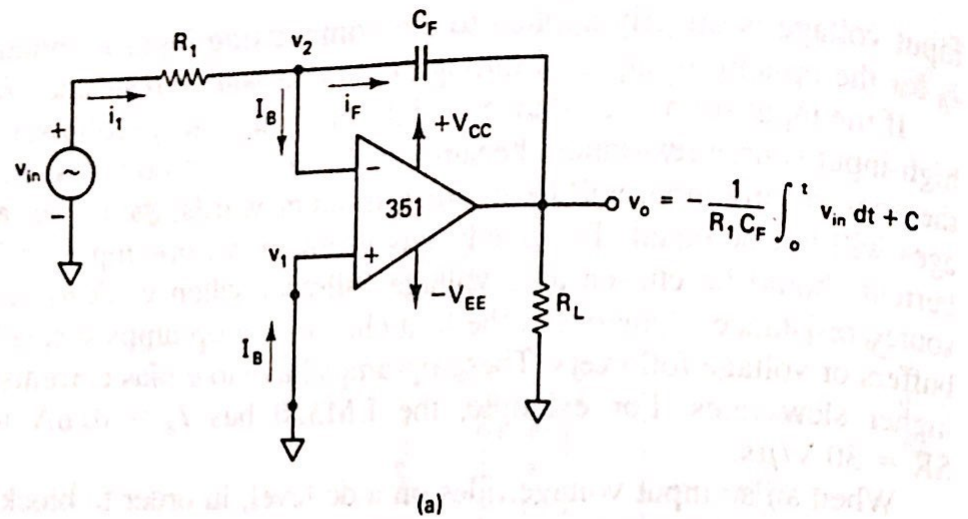


FIGURE 6-23 (a) The integrator circuit. (b) and (c) Input and ideal output waveforms using a square wave and sine wave, respectively. $R_1 C_F = 1$ second and $V_{\infty T} = 0$ V

Therefore,

$$\frac{v_{in} - v_2}{R_1} = C_F \left(\frac{d}{dt} \right) (v_2 - v_o)$$

However, $v_1 = v_2 \cong 0$ because A is very large. Therefore,

$$\frac{v_{in}}{R_1} = C_F \frac{d}{dt} (-v_o)$$

The output voltage can be obtained by integrating both sides with respect to time:

$$\begin{aligned} \int_0^t \frac{v_{in}}{R_1} dt &= \int_0^t C_F \frac{d}{dt} (-v_o) dt \\ &= C_F (-v_o) + v_o|_{t=0} \end{aligned}$$

Therefore,

$$v_o = -\frac{1}{R_1 C_F} \int_0^t v_{in} dt + C \quad (6-23)$$

where C is the integration constant and is proportional to the value of the output voltage v_o at time $t = 0$ seconds.

Equation (6-23) indicates that the output voltage is directly proportional to the negative integral of the input voltage and inversely proportional to the time constant $R_1 C_F$. For example, if the input is a sine wave, the output will be a cosine wave; or if the input is a square wave, the output will be a triangular wave, as shown in Figure 6-23(c) and (b), respectively. Note that these waveforms are drawn with the assumption that $R_1 C_F = 1$ second and $V_{ooT} = 0$ V; that is, $C = 0$.

When $v_{in} = 0$, the integrator of Figure 6-23(a) works as an open-loop amplifier. This is because the capacitor C_F acts as an open circuit ($X_{CF} = \infty$) to the input offset voltage V_{io} . In other words, the input offset voltage V_{io} and the part of the input current charging capacitor C_F produce the error voltage at the output of the integrator. Therefore, in the practical integrator shown in Figure 6-25, to reduce the error voltage at the output, a resistor R_F is connected across the feedback capacitor C_F . Thus, R_F limits the low-frequency gain and hence minimizes the variations in the output voltage.

The frequency response of the basic integrator is shown in Figure 6-24. In this figure, f_b is the frequency at which the gain is 0 dB and is given by

$$f_b = \frac{1}{2\pi R_1 C_F} \quad (6-24)$$

For the derivation of Equation (6-24), refer to Appendix C.

Both the stability and the low-frequency roll-off problems can be corrected by the addition of a resistor R_F as shown in the *practical integrator* of Figure 6-25. The term stability refers to a constant gain as frequency of an input signal is varied over a certain range. Also, low-frequency roll off refers to the rate of decrease in gain at lower frequencies. The frequency response of the practical

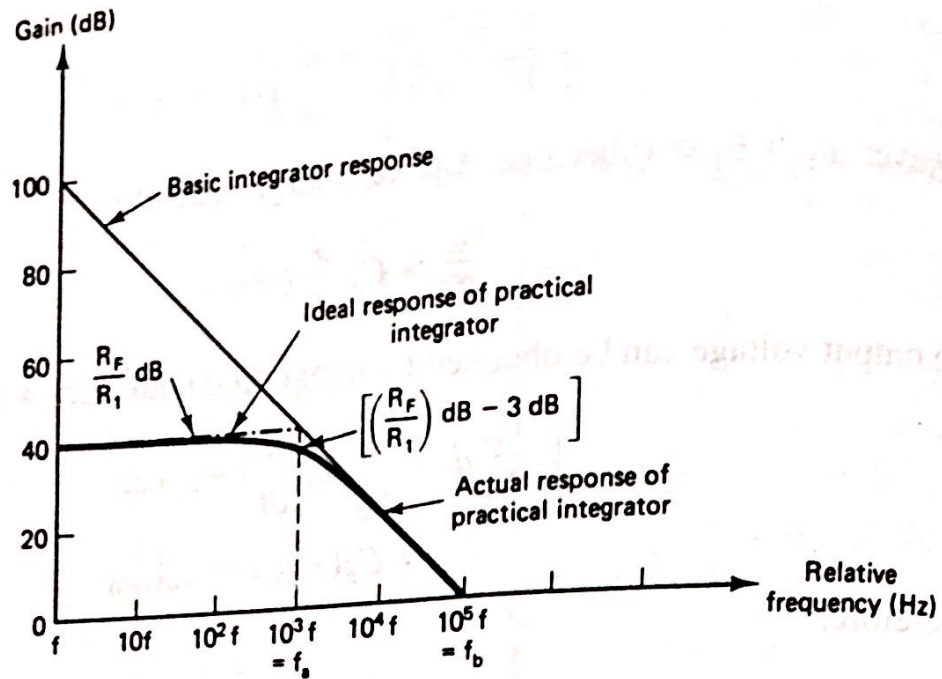


FIGURE 6-24 Frequency response of basic and practical integrators. $f_a = 1/(2\pi R_F C_F)$ and $f_b = 1/(2\pi R_1 C_F)$.

integrator is shown in Figure 6-24 by a dashed line. In this figure, f is some relative operating frequency, and for frequencies f to f_a to gain R_F/R_1 is constant. However, after f_a the gain decreases at a rate of 20 dB/decade. In other words, between f_a and f_b the circuit of Figure 6-25 acts as an integrator. The gain-limiting frequency f_a is given by

$$f_a = \frac{1}{2\pi R_F C_F} \quad (6-25)$$

Refer to Appendix C for derivation.

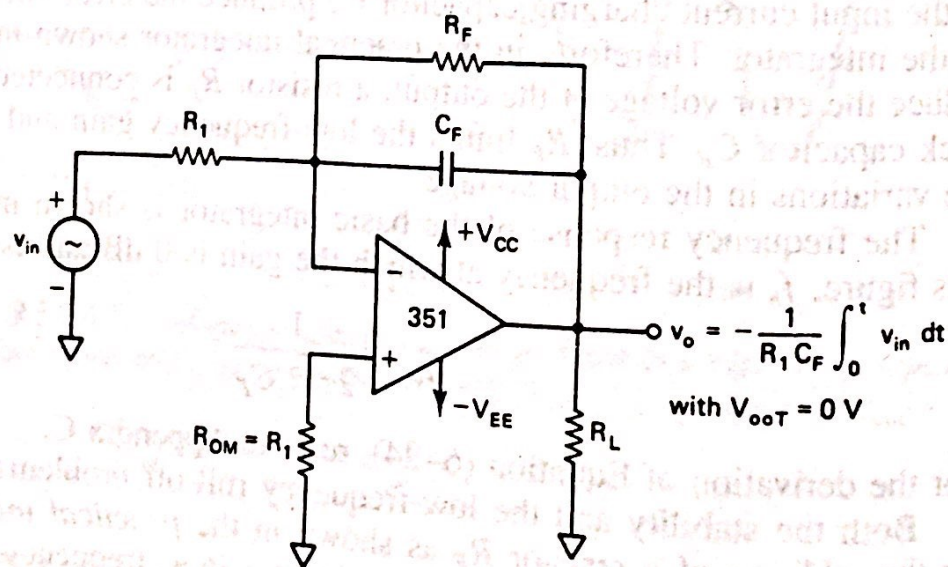


FIGURE 6-25 Practical integrator.

Generally, the value of f_a and in turn R_1C_F and R_FC_F values should be selected such that $f_a < f_b$. For example, if $f_a = f_b/10$, then $R_F = 10R_1$. In fact, the input signal will be integrated properly if the time period T of the signal is larger than or equal to R_FC_F . That is,

$$T \geq R_FC_F \quad (6-26)$$

where

$$R_FC_F = \frac{1}{2\pi f_a}$$

The integrator is most commonly used in analog computers and analog-to-digital (ADC) and signal-waveshaping circuits.

6-13 THE DIFFERENTIATOR

Figure 6-27(a) shows the *differentiator* or *differentiation amplifier*. As its name implies, the circuit performs the mathematical operation of differentiation; that is, the output waveform is the derivative of the input waveform. The differentiator may be constructed from a basic inverting amplifier if an input resistor R_1 is replaced by a capacitor C_1 .

The expression for the output voltage can be obtained from Kirchhoff's current equation written at node v_2 as follows:

$$i_C = I_B + i_F$$

Since $I_B \cong 0$,

$$i_C = i_F$$

$$C_1 \frac{d}{dt} (v_{in} - v_2) = \frac{v_2 - v_o}{R_F}$$


But $v_1 = v_2 \cong 0$ V, because A is very large. Therefore,

$$C_1 \frac{dv_{in}}{dt} = - \frac{v_o}{R_F}$$


or

$$v_o = -R_F C_1 \frac{dv_{in}}{dt} \quad (6-27)$$

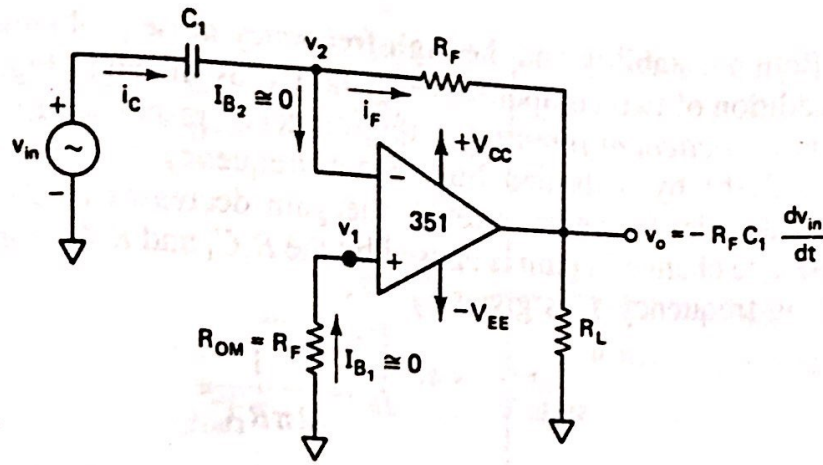Thus the output v_o is equal to $R_F C_1$ times the negative instantaneous rate of change of the input voltage v_{in} with time. Since the differentiator performs the reverse of the integrator's function, a cosine wave input will produce a sine wave output, or a triangular input will produce a square wave output. However, the differentiator



(a)

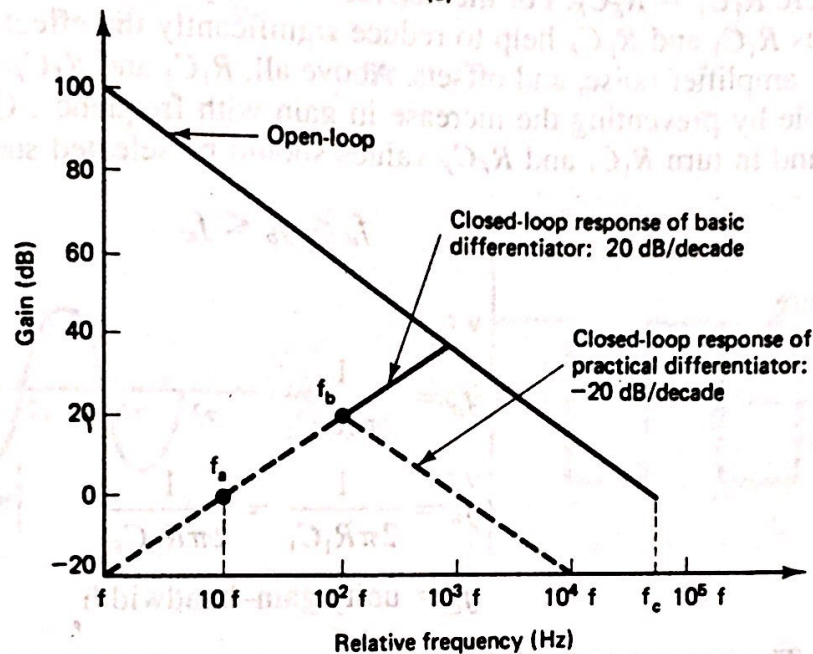

(b)

FIGURE 6-27 Basic differentiator. (a) Circuit. (b) Frequency response.

of Figure 6-27(a) will not do this because it has some practical problems. The gain of the circuit (R_F/X_{C1}) increases with increase in frequency at a rate of 20 dB/decade. This makes the circuit unstable. Also, the input impedance X_{C1} decreases with increase in frequency, which makes the circuit very susceptible to high-frequency noise. When amplified, this noise can completely override the differentiated output signal. The frequency response of the basic differentiator is shown in Figure 6-27(b). In this figure, f_a is the frequency at which the gain is 0 dB and is given by

$$f_a = \frac{1}{2\pi R_F C_1} \quad (6-28)$$

Also, f_c is the unity gain-bandwidth of the op-amp, and f is some relative operating frequency. For the derivation of Equation (6-28), refer to Appendix C.

Both the stability and the high-frequency noise problems can be corrected by the addition of two components: R_1 and C_F , as shown in Figure 6-28(a). This circuit is a *practical differentiator*, the frequency response of which is shown in Figure 6-27(b) by a dashed line. From frequency f to f_b , the gain increases at 20 dB/decade. However, after f_b the gain decreases at 20 dB/decade. This 40-dB/decade change in gain is caused by the R_1C_1 and R_FC_F combinations. The gain-limiting frequency f_b is given by

$$f_b = \frac{1}{2\pi R_1 C_1} \quad (6-29)$$

where $R_1C_1 = R_FC_F$. For the derivation of Equation (6-29), refer to Appendix C. Thus R_1C_1 and R_FC_F help to reduce significantly the effect of high-frequency input, amplifier noise, and offsets. Above all, R_1C_1 and R_FC_F make the circuit more stable by preventing the increase in gain with frequency. Generally, the value of f_b and in turn R_1C_1 and R_FC_F values should be selected such that

$$f_a < f_b < f_c \quad (6-30)$$

where

$$f_a = \frac{1}{2\pi R_F C_1}$$

$$f_b = \frac{1}{2\pi R_1 C_1} = \frac{1}{2\pi R_F C_F}$$

$$f_c = \text{unity gain-bandwidth,}$$


The input signal will be differentiated properly if the time period T of the input signal is larger than or equal to R_FC_1 . That is,

$$T \geq R_FC_1$$




Figure 6-28(b) and (c) show the sine wave and square wave inputs and resulting differentiated outputs, respectively, for the practical differentiator. A workable differentiator can be designed by implementing the following steps (see Example 6-16):

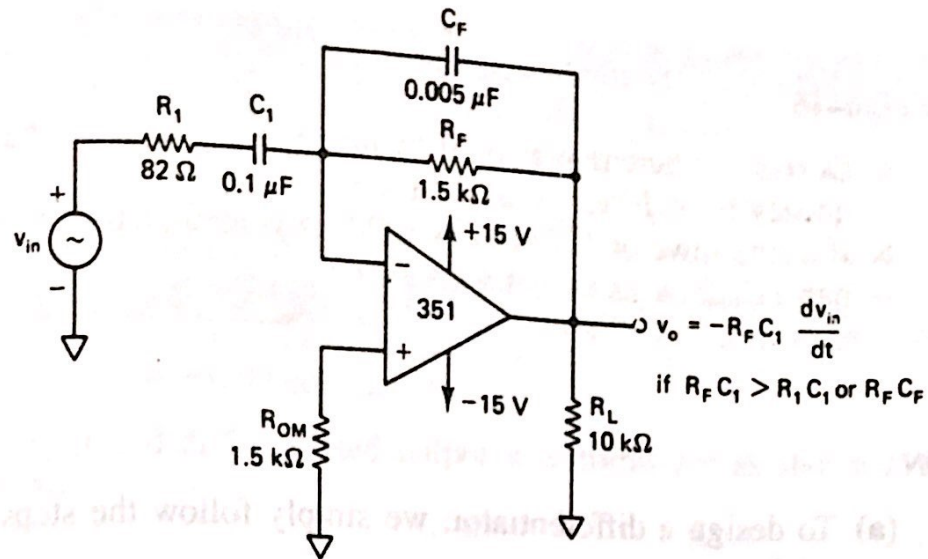1. Select f_a equal to the highest frequency of the input signal to be differentiated. Then, assuming a value of $C_1 < 1 \mu\text{F}$, calculate the value of R_F .
2. Choose $f_b = 20f_a$ and calculate the values of R_1 and C_F so that $R_1C_1 = R_FC_F$.


The differentiator is most commonly used in waveshaping circuits to detect high-frequency components in an input signal and also as a rate-of-change detector in FM modulators.



(a)

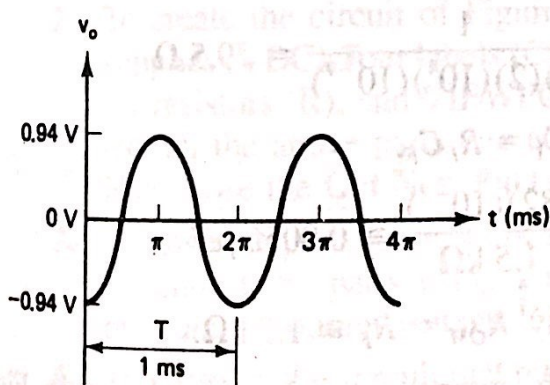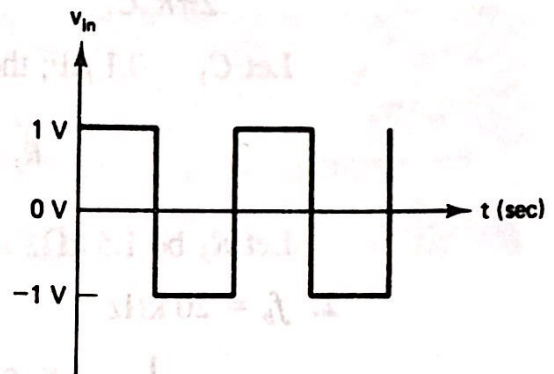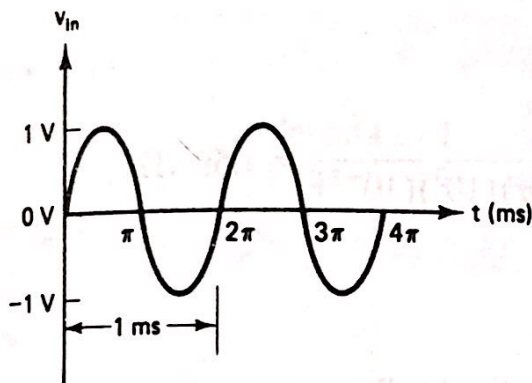

(b)

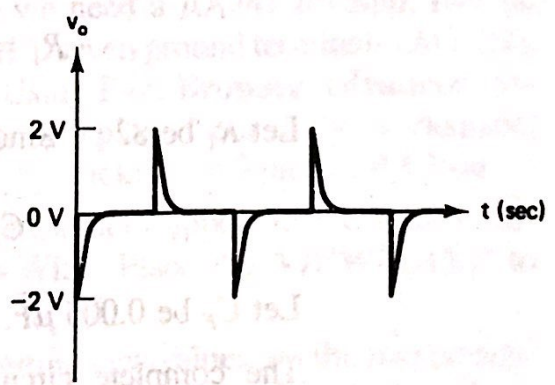

(c)

FIGURE 6-28 Practical differentiator. (a) Circuit. (b) Sine wave input and resulting cosine wave output. (c) Square wave input and resulting spike output.